 


# Ch 5 - Sequential Logic



# Digital State



- memory stores current state, produced at output
- combinational logic computed.
  - next state
  - output bits
- State changes on Load control input

# Memory : Capacitors vs Feedback

Capacitors

Pros

- compact / low cost

Cons

- complex interface

- leaks

To write:

↳ drive bit line

↓  
turn on access fet

↓  
force storage cap  
to a new voltage

To read:

↳ precharge bit line

↓  
turn on access fet


↓  
detect small  
change in bit  
line voltage

Feedback

↳ use positive  
feedback to store  
indefinitely  
↳ bistable storage


three solutions:

 ↳ two endpoints are stable  
↳ middle point is metastable



 
# Settable Memory Element

↳ it's easy to build settable storage element (latch) using a 1-bit MUX



← D-Latch


 
$D$ : data input  
 $G$ : gate input  
 $Q$ : state output



Output valid when:

- ↳  $G=1$ ,  $D$  stable for  $T_{PD}$ , independently of  $Q'$
- ↳  $Q=0$  stable for  $T_{PD}$ , independently of  $G$
- ↳  $G=0$ ,  $Q$  stable for  $T_{PD}$ , independently of  $D$

# D-Register

  

↳ master closed when slave open (vice-versa)  
 ↳ implies no combinational path through register

↳ timing


↳  $t_{PD} : CLK \rightarrow Q$

↳  $t_{CD} : CLK \rightarrow Q$

↳  $t_{SETUP}$  : guarantees D has propagated through feedback path before master has closed

↳  $t_{HOLD}$  : guarantees master is closed and data is stable before allowing D to change

# Single-Clock Synchronous Circuit

 

register  $\rightarrow$  building block

- $\rightarrow$  no combinational cycles
- $\rightarrow$  single periodic clock signal shared among all clocked devices
- $\rightarrow$  only care about value of register data inputs just before rising edge of clock
- $\rightarrow$  period greater than every combinational delay + setup time
- $\rightarrow$  change saved state after noise-inducing logic transitions have stopped